

## Homework - I (B)

ANUBHAV BHATLA

200070008

$M$  attains two values : 0 and 1

- (i)  $M = 0$  : The output of the first XOR gate is  $B_0$ .  
Thus the output of the first Full Adder,  $S_0$  is  $A_0 + B_0$ .  
Similarly for the other 3 Full Adders.  
Thus we get the final output  $A + B$ .  
∴ The circuit behaves as a 4 bit Adder.

- (ii)  $M = 1$  : The output of the first XOR gate is  $B'_0$  (complement of  $B_0$ ). Thus the output of the first Full Adder is  $A_0 + B'_0 + M = A_0 + B'_0 + 1$ . This is equal to  $A_0 - B_0$ . Similarly for the other 3 Full Adders.  
Thus we get the final output  $A - B$ .  
∴ The circuit behaves as a 4 bit Subtractor.